

Electronika 13.0 Solutions

1

Question

You have been recruited by a company that manufactures CPUs. The task of developing a prototype ALU for an upcoming CPU is given to you. The CPU is meant to work with signed (2's complement) 8-bit numbers. An ALU has several control signals that select what operation is to be performed. The design specifications are as follows:

Name	Type	Size	Description
PRIMARY INPUTS			
x	Input	8-bit, signed	Operand 1
y	Input	8-bit, signed	Operand 2
PRIMARY OUTPUT			
out	Output	8-bit, signed	Final result after computation
CONTROL SIGNALS			
nx	Input	1-bit	If set, perform 2's complement of the operand 'x'
ny	Input	1-bit	If set, perform 2's complement of the operand 'y'
f	Input	1-bit	If set, perform 'x + y' (addition), else perform 'x AND y'
FLAGS			
zr	Output	1-bit	If 'out' is zero, set to '1', else set to '0'
ng	Output	1-bit	If 'out' is negative, set to '1', else set to '0'

The ALU must be able to produce the following outputs making use of the different control signals:

- $x + y$
- $x - y$
- $y - x$
- $x \text{ AND } y$

Also, provide a truth table for the control signals and the output they produce.

Answer

You can find the simulation [here](#)

Control signal table:

nx	ny	f	out
0	0	1	$x + y$
0	1	1	$x - y$
1	0	1	$y - x$
0	0	0	$x \text{ AND } y$

PTO.

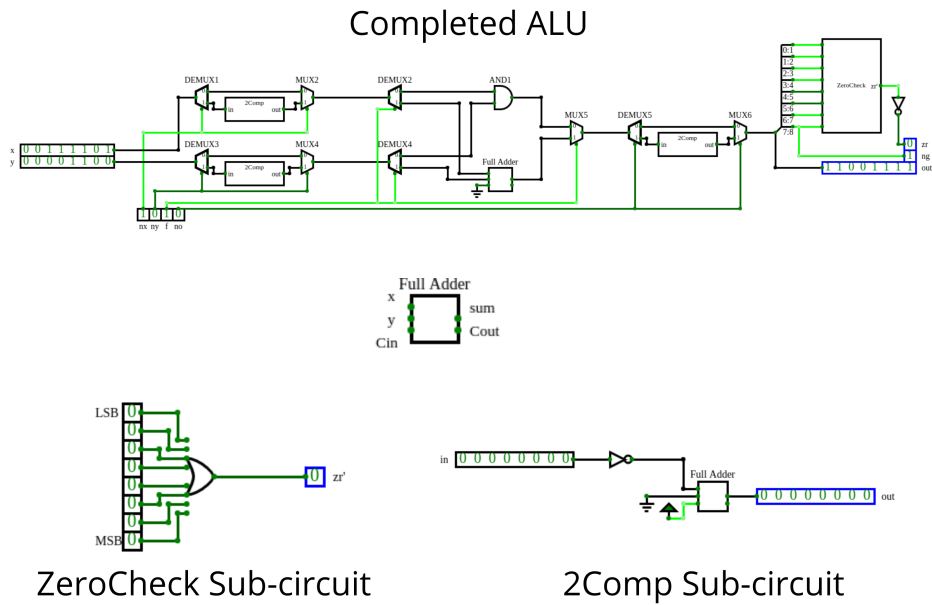


Figure 1: Electronika ALU

2

Question

For the given circuit, what will be the state of each flip-flop after 4 clock cycles(enter 4 bit binary answer)?

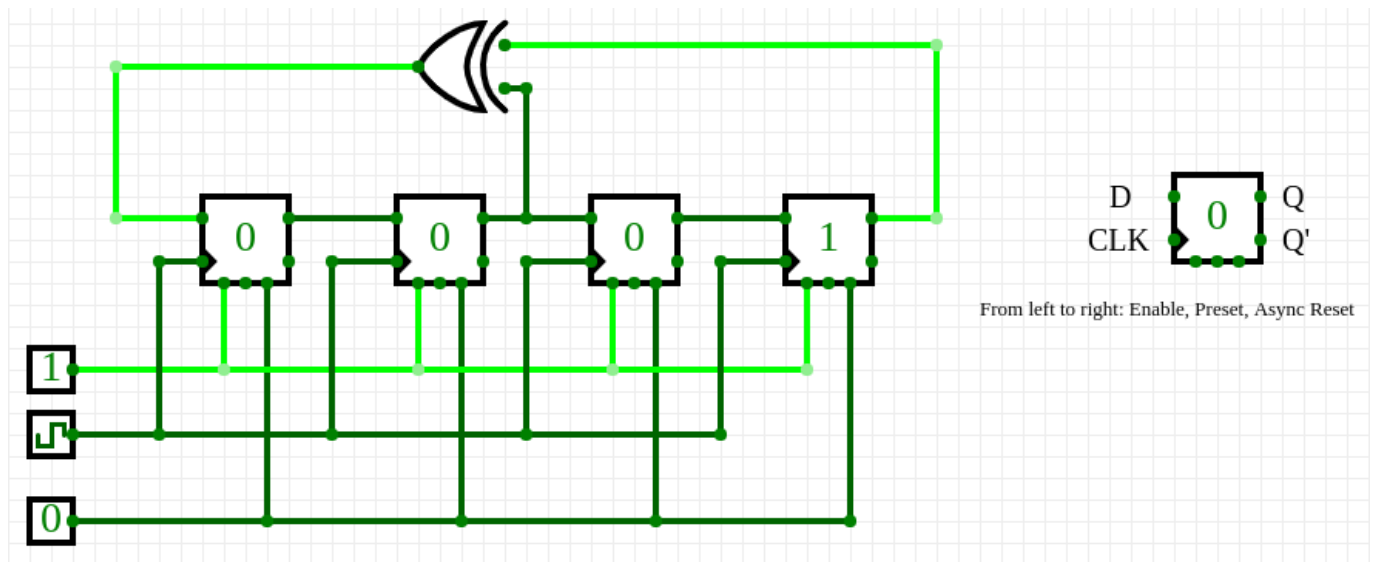


Figure 2: Linear Feedback Shift Register (LFSR)

Answer

0101

You can find the simulation [here](#)

3

Question

What is the parity bit for the word 1101010100001011?

Answer

0

4

Question

You are trying to reverse engineer a logic board. You see that a couple of lines that you are probing give the following output on an oscilloscope. Decipher what protocol is being used and what message is being sent.

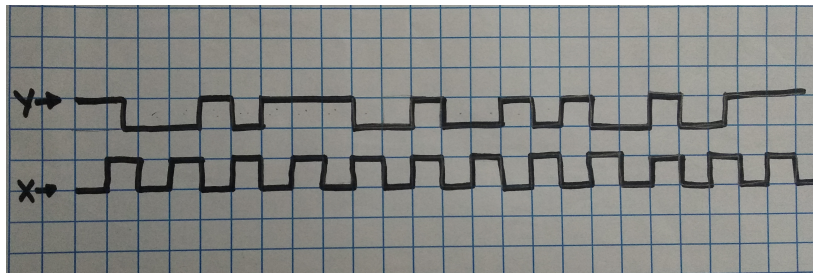


Figure 3: I2C probe

Answer

I2C protocol, 00101001

'X' is the SCL line and 'Y' is the SDA line

5

Question

Represent the given 8-bit numbers in the Big-Endian format, given a word-length of 4 bits: 11010111, 00101101 (answer must be comma-separated values of each row)

Answer

1101, 0111, 0010, 1101

In memory, it would look like this:

Address 0	1101
Address 1	0111
Address 2	0010
Address 3	1101

6

Question

Identify the logic function of the following circuit

PTO.

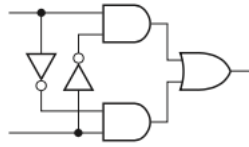


Figure 4: Logic circuit

Answer

XOR

7

Question

Guess the component: It is used to attenuate high-frequency electromagnetic interference (EMI) in a circuit. It works like a low pass filter that allows only low-frequency signals to pass through a circuit and eliminates the high-frequency noise.


Answer

Ferrite bead


8

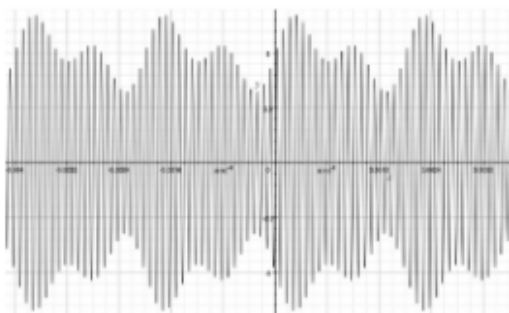Question

To obtain the output waveform 'Y' from the input waveform 'X,' design the circuit block 'A'



X

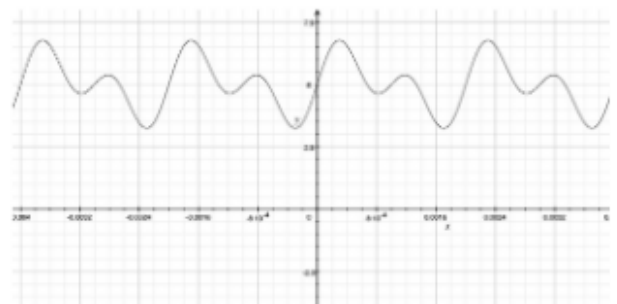

Y

Figure 5: Modulation

Answer

The technique used is amplitude modulation (AM), and requires an envelope detector along with a low-pass filter for demodulation.

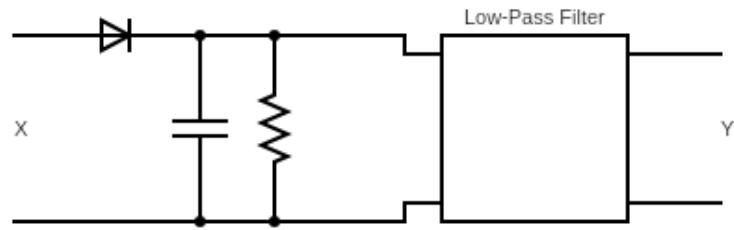


Figure 6: Envelope detector

9

Question

Determine the type of filter from the following transfer function:

$$T(s) = a \frac{(s^2 + \omega_n^2)}{(s^2 + s \frac{\omega_0}{Q} + \omega_0^2)} \quad (\omega_n \geq \omega_0)$$

Answer

Low-pass notch filter

10

Question

What is the output voltage ' V_o ' of the circuit if the input voltage is 5 V?

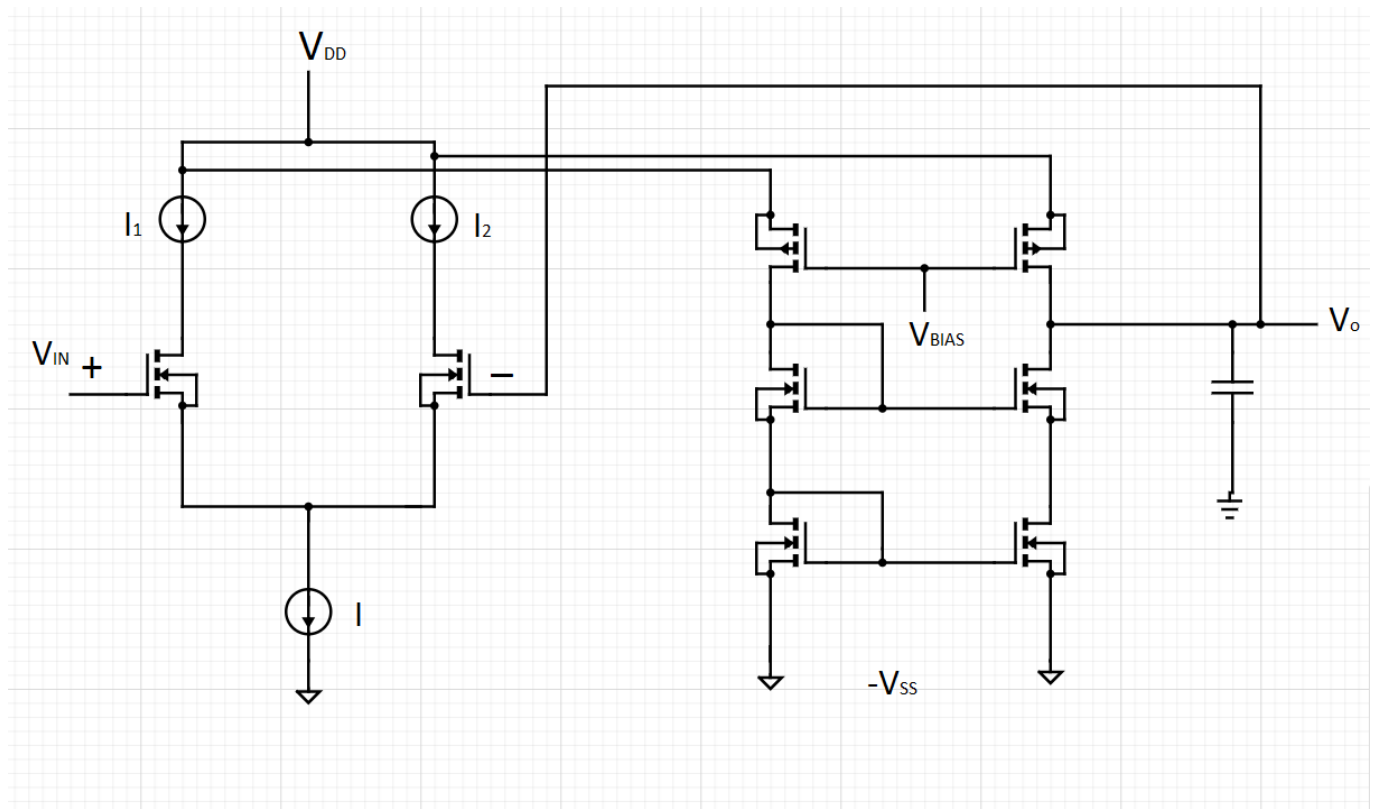


Figure 7: MOSFET circuit

Answer


5 V

This is an op-amp that is wired up as a voltage follower.

11

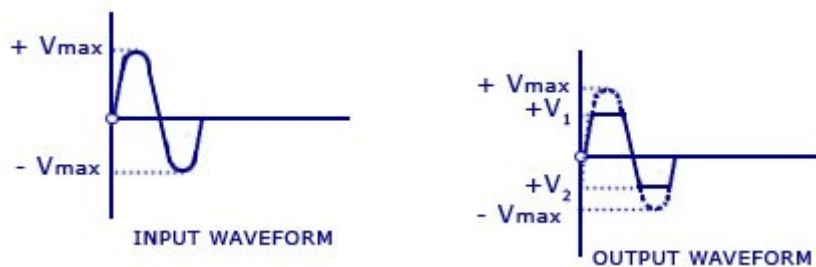Question

Given the input, which of the following circuits gives the required output?



Answer

A biased, double-ended clipper is needed to produce the given output.

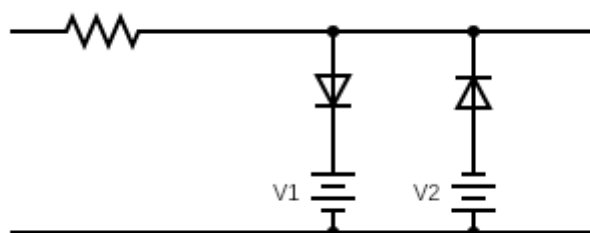


Figure 8: Clipper

PTO.

12

Question

Find the output voltage of the circuit shown below.

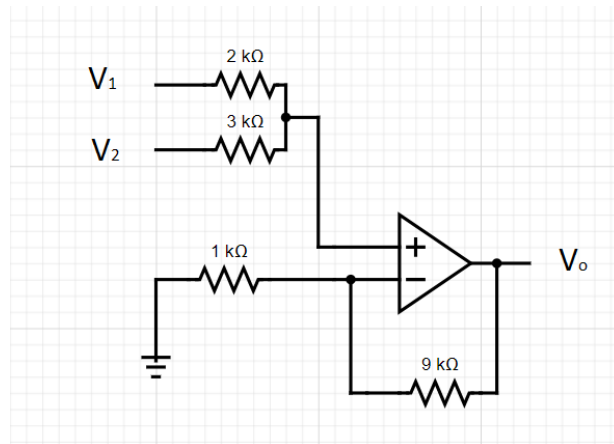


Figure 9: Op-amp circuit

Answer

$$6V_1 + 4V_2$$

13

Question

Design a filter using an op-amp for the given transfer function:

$$T(s) = -a \frac{(s - \omega_0)}{(s + \omega_0)}$$

Answer

The filter is an all-pass filter

$$\text{Here, } RC = \frac{1}{\omega_0}$$

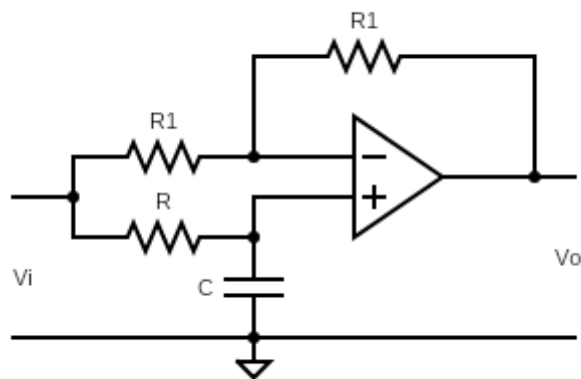


Figure 10: Filter

14

Question

Construct a CMOS logic circuit that realises the given truth table.

A	B	C	Output
F	F	F	T
F	F	T	T
F	T	F	T
F	T	T	F
T	F	F	F
T	F	T	F
T	T	F	F
T	T	T	F

Answer

The simplified boolean expression is $A'B' + A'C'$ which is equivalent to $(A + BC)'$

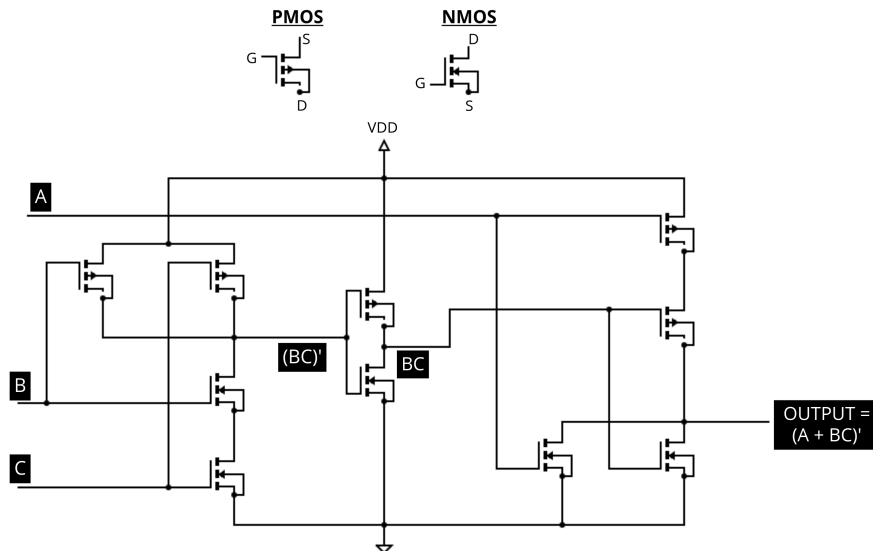


Figure 11: CMOS Logic Circuit

15

Question

Simplify the Boolean expression $Y = A'B'C' + A'B'C + A'BC' + AB'C' + ABC'$

Answer

$$Y = A'B' + C'$$

16

Question

What are the three essential components required for high voltage switching using MCUs?

Answer

Optocoupler, Darlington transistor, Relay

17

Question

Consider a 4 bit Johnson counter with an initial value of 0111. What is the counting sequence of this counter? (Answer in decimal)

Answer

7, 3, 1, 0, 8, 12, 14, 15, 7

18

Question

Rahul has just realized that polynomial multiplication is just the linear convolution of the coefficients. Help him build a hardware circuit for performing linear convolution using a hardware description language.

Answer

This solution is written in Verilog HDL. It is a module that performs linear convolution on two 8-bit numbers.

```
module linear_convolution(A,B,R);

    input [7:0] A, B;
    output [15:0] R;

    wire A0, A1, A2, A3, A4, A5, A6, A7;
    wire B0, B1, B2, B3, B4, B5, B6, B7;
    wire C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12, C13, C14;
    wire R0, R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14;

    assign A0 = A[0];
    assign A1 = A[1];
    assign A2 = A[2];
    assign A3 = A[3];
    assign A4 = A[4];
    assign A5 = A[5];
    assign A6 = A[6];
    assign A7 = A[7];

    assign B0 = B[0];
    assign B1 = B[1];
    assign B2 = B[2];
    assign B3 = B[3];
    assign B4 = B[4];
    assign B5 = B[5];
    assign B6 = B[6];
    assign B7 = B[7];

    assign R0 = A0 && B0 ;
    assign {C1, R1} = (A0 & B1) + (A1 & B0); // Continued on next page
```

```

assign {C2, R2} = C1 + (A0 && B2) + (A2 && B0) + (A1 && B1);
assign {C3, R3} = C2 + (A3 && B0) + (A0 && B3) + (A1 && B2) + (A2 && B1);
assign {C4, R4} = C3 + (A4 && B0) + (A0 && B4) + (A3 && B1) + (A1 && B3) + (A2 && B2);
assign {C5, R5} = C4 + (A5 && B0) + (A0 && B5) + (A4 && B1) + (A1 && B4) + (A3 && B2) + (A2 && B3);
assign {C6, R6} = C5 + (A6 && B0) + (A0 && B6) + (A5 && B1) + (A1 && B5) + (A4 && B2) + (A2 && B4) + (A3 && B3);
assign {C7, R7} = C6 + (A7 && B0) + (A0 && B7) + (A6 && B1) + (A1 && B6) + (A5 && B2) + (A2 && B5) + (A4 && B3) + (A3 && B4);
assign {C8, R8} = C7 + (A7 && B1) + (A1 && B7) + (A6 && B2) + (A2 && B6) + (A5 && B3) + (A3 && B5) + (A4 && B4);
assign {C9, R9} = C8 + (A7 && B2) + (A2 && B7) + (A6 && B3) + (A3 && B6) + (A5 && B4) + (A4 && B5);
assign {C10, R10} = C9 + (A7 && B3) + (A3 && B7) + (A6 && B4) + (A4 && B6) + (A5 && B5);
assign {C11, R11} = C10 + (A7 && B4) + (A4 && B7) + (A6 && B5) + (A5 && B6);
assign {C12, R12} = C11 + (A7 && B5) + (A5 && B7) + (A6 && B6);
assign {C13, R13} = C12 + (A7 && B6) + (A6 && B7);
assign {C14, R14} = C13 + (A7 && B7);
endmodule

```

19

Question

Fibonacci numbers are incredibly easy to understand for right? Well here is a new challenge! Design a digital circuit that generates all the Fibonacci numbers between 0 and 15.

Answer

The required sequence is 0, 1, 2, 3, 5, 8, 13, since we are not asking for the Fibonacci series, but only the numbers. Since the largest number- 13 requires 4 bits, 4 flip-flops are required. T flip-flops are used in this solution. Let us call them T_3 , T_2 , T_1 , T_0 (T_3 is the MSB and T_0 is the LSB). Similarly, their outputs are Q_3 , Q_2 , Q_1 , Q_0 respectively.

Present State				Next State			
Q_3	Q_2	Q_1	Q_0	Q_3^+	Q_2^+	Q_1^+	Q_0^+
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	1
0	1	0	1	1	0	0	0
1	0	0	0	1	1	0	1
1	1	0	1	0	0	0	0

The inputs of each flip-flop for each count are obtained using the transition table of the T flip-flop


T_3	T_2	T_1	T_0
0	0	0	1
0	0	1	1
0	0	0	1
0	1	1	0
1	1	0	1
0	1	0	1
1	1	0	1

Using K-maps for T_n , we can calculate the individual flip-flop inputs.

T_3	T_2	T_1	T_0
Q_2	$Q_2 + Q_3 + (Q_1 \cdot Q_0)$	$Q_2' \cdot Q_0$	$Q_1' + Q_0'$

You can find the simulation [here](#)

PTO.

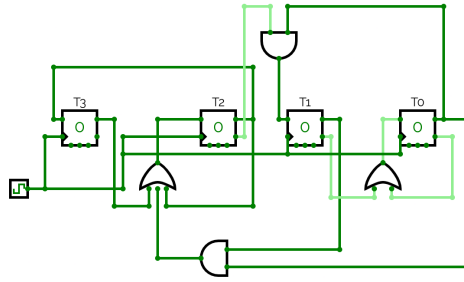

20

Question

Rahul is an Embedded Software developer. He was given two code snippets at work, both of them perform the same function. Help him figure out what they do.

ARM

```

AREA Program, CODE, READONLY
ENTRY
Main

    LDR    R0, =Value1
    LDR    R1, [R0]
    LDR    R2, [R0, #4]
    LDR    R0, =Value2
    LDR    R3, [R0]
    LDR    R4, [R0, #4]
    ADDS   R6, R2, R4
    ADC    R5, R1, R3
    LDR    R0, =Result
    STR    R5,[R0]
    STR    R6, [R0, #4]
    SWI    &11

Value1 DCD &12A2E640, &F2100123
Value2 DCD &001019BF, &40023F51
Result DCD 0

END

```

x86

```
data segment
a dq 10000 ;in hex 2701h
b dq 10000 ;in hex 2701h
c dq ?
data ends

code segment
assume cs:code, ds:data
start:
mov ax,data
mov ds,ax
lea si,a
lea di,b
lea bx,c

mov ax,[si]
add ax,[di]
mov [bx],ax

mov ax,[si+2]
adc ax,[di+2]
mov [bx+2],ax

mov ax,[si+4]
adc ax,[di+4]
mov [bx+4],ax

mov ax,[si+6]
adc ax,[di+6]
mov [bx+6],ax

mov ah,4ch
int 21h
code ends
end start
```

Figure 13: Snippets

Answer

Both programs perform the addition of two 64-bit numbers.

21

Question

Rahul found an old-tech memory solution that he knows how to write, but he's not sure how to read the written data. Help him find written data.

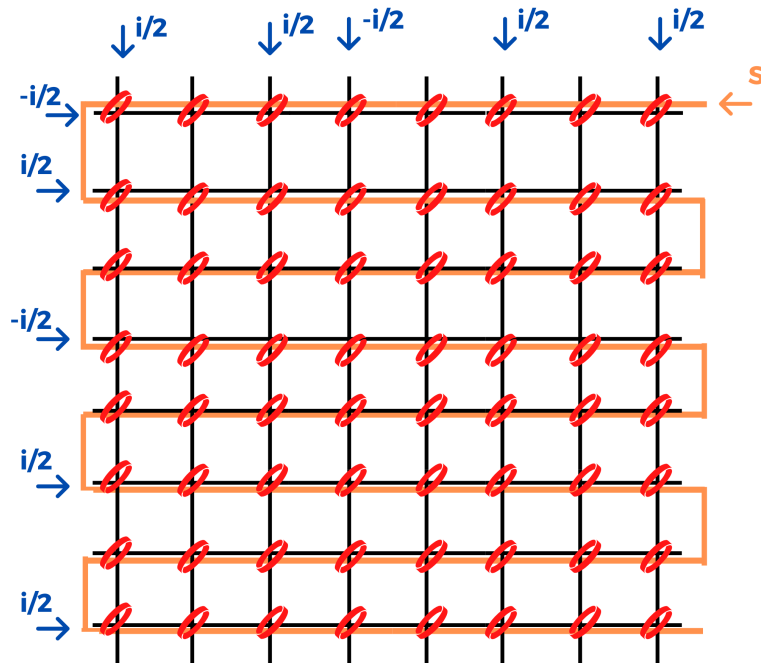


Figure 14: Memory

Answer

The figure represents a variation of “[Ferrite core memory](#)”. This is technology from the 1950’s, and was famously used for the computers on NASA’s Saturn V rocket! Each ring represents a single bit of information, so here, there are 64 bits of data. If the currents flowing into a ring add up to i , then a logical 1 is stored, otherwise, a logical 0 is stored.

The data stored is as follows (row-wise, from top to bottom)-

0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	1
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	1
0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	1

22

Question

Can a 16-bit timer be realized using an 8-bit timer on an AVR microcontroller (e.g. ATMEGA328p)? If yes, how?

Answer

Yes, it can be done. **PTO.**

```

// This sample program creates delay of 1 second on an ATMEGA328p
// 'reg' is a soft(ie it is not part of the hardware) 8-bit register
union reg {
    struct bitsy {
        unsigned int b0: 1;
        unsigned int b1: 1;
        unsigned int b2: 1;
        unsigned int b3: 1;
        unsigned int b4: 1;
        unsigned int b5: 1;
        unsigned int b6: 1;
        unsigned int b7: 1;
    } bits;
    int bytes: 8;
} x;

void init(int ocr) {
    DDRB |= (1 << PB5);
    cli();
    OCR0A = ocr;
    TCCR0A |= (1 << WGM01) | (1 << COM0A0);
    TCCR0B |= (1 << CS02) | (1 << CS00);
    TIMSK0 |= (1 << OCIE0A);
    sei();
}

void start(int millies) {
    int temp = 0;
    if (millies < 256) {
        init(millies);
    }
    else {
        temp = ceil(millies / 255.0);
        x.bytes = temp;

        while (x.bytes > 0) {
            init(255);
        }
    }
}

int main() {
    while (1) {
        start(17000);
        PORTB ^= (1 << PB5);
    }
}

ISR(TIMER0_COMPA_vect) {
    x.bytes -= 1;
}

```

23

Question

Rahul wants to read and analyze heartbeat signals. Since heartbeat signals are very low-level signals, help him design a differential amplifier with a high CMRR, high gain, and high accuracy. The amplifier must provide a gain that can be varied over the range of 2 to 1000 using a 100 k Ω potentiometer.

PTO.

Answer

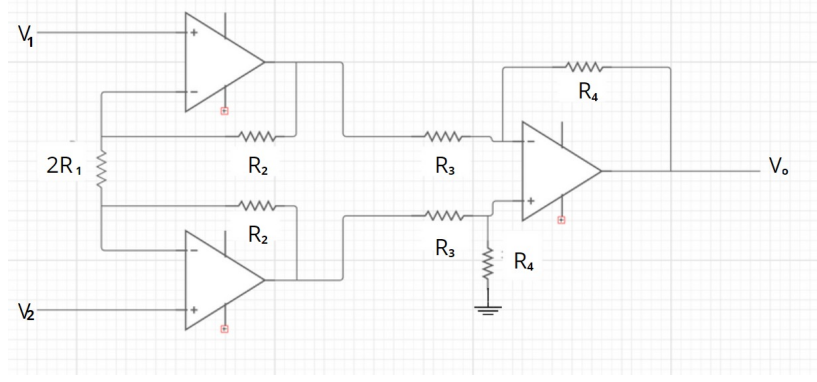


Figure 15: Instrumentation amplifier

An instrumentation amplifier is required for this purpose (Why? because we require high CMRR, gain and accuracy). The input voltages are taken via electrodes on the skin, or through photo-transistors and an IR LED placed near the skin. As shown in the figure, it is built in two stages. In the first stage, $2R_1$ is taken as the series combination of a fixed resistance R_{1f} and a variable resistance R_{1v} . The $100\text{ k}\Omega$ potentiometer is used as R_{1v} .

$$2R_1 = R_{1f} + R_{1v}$$

The second stage is usually kept at unity gain, therefore we can select the values of R_3 and R_4 to be any practically convenient value, say $10\text{ k}\Omega$. The equivalent gain of both stages combined is their product, so if the gain of the first stage is G , the overall gain is $G \times 1$. Thus the entire gain of the amplifier is provided by the first stage itself.

It is given that $2 \leq G \leq 1000$

$$\text{The gain of the first stage is given by } G = 1 + \frac{2R_2}{R_{1f} + R_{1v}}$$

For maximum gain(i.e. 1000), take $R_{1v} = 0\text{ }\Omega$ (minimum R)

$$1 + \frac{2R_2}{R_{1f}} = 1000 \quad (1)$$

For minimum gain(i.e. 2), take $R_{1v} = 100\text{ k}\Omega$ (maximum R)

$$1 + \frac{2R_2}{R_{1f} + 100\text{ k}\Omega} = 2 \quad (2)$$

On solving equations (1) and (2), we get $R_{1f} = 100.2\text{ }\Omega$ and $R_2 = 50.050\text{ k}\Omega$

Therefore, the entire design is as follows:

Resistance	Value
R_{1f}	$100.2\text{ }\Omega$
R_{1v}	$0\text{ }\Omega$ to $100\text{ k}\Omega$
R_2	$50.050\text{ k}\Omega$
R_3	$10\text{ k}\Omega$
R_4	$10\text{ k}\Omega$